


Lab 2

2 Bit Comparator

Errors in Code:

1. Missing semicolon on line 15 in eq2.v.
2. Line 15 in eq2.v had the arguments in the wrong order. Fixed these so that the two test bits are first and then the output bit.
3. Line 18 in eq2.v had the wrong operator for comparison. Changed the line to use the AND operator rather than the XOR operator.
4. Changed eq3 to eq1

Corrected Simulation Output

 

Output in TCL console after using the “\$monitor” command:

```
Vec 1: 00, Vec 2: 00, Output: 1
Vec 1: 01, Vec 2: 00, Output: 0
Vec 1: 01, Vec 2: 11, Output: 0
Vec 1: 10, Vec 2: 10, Output: 1
Vec 1: 10, Vec 2: 00, Output: 0
Vec 1: 11, Vec 2: 11, Output: 1
```

No it is not adequate testing since it doesn't run through all the possible permutations of the inputs. We can't take for granted that the output from (01, 10) will be the same as (10, 01).

2 Bit Greater than Circuit


Truth Table: (Testing if Vec0 > Vec1)

Test Vector 0		Test Vector 1		Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Minimized SOP:

$$y = AC' + BC'D' + ABD'$$

Output after Simulation:

 

Test Vectors:

Used a nested for loop in Verilog to run through all possible permutations for the two bit comparator. This is sufficient as it exhaustively tests all possible permutations.

For the greater than or equal to circuit, the two bit modules were instantiated and then connected together using a series of gates.

2 Bit Equal Module Verilog Code

// Listing 1.4

```
module eq2
(
    input  wire[1:0] a, b,                // a and b are the two 2-bit numbers to compare
    output wire aeqb                      // single bit output. Should be high if a and b are the same
);

    // internal signal declaration, used to wire outputs of the 1 bit comparators
    wire e0, e1;

    // body
    // instantiate two 1-bit comparators that we already know are tested and work
    // named instantiation allows us to change order of ports.
    eq1 eq_bit0_unit (.i0(a[0]), .i1(b[0]), .eq(e0));
    eq1 eq_bit1_unit (.i0(a[1]), .i1(b[1]), .eq(e1));

    // a and b are equal if individual bits are equal, which comes from the 1-bit comparators
    assign aeqb = e0 & e1;
endmodule
```

2 Bit Greater Than

`timescale 1ns / 10ps

//2 bit Comparator Module. Checks if in0 > in1. Return 1 if true. 0 otherwise.

module bit2_GTH(input wire [1:0] in0, input wire [1:0] in1, output wire comp);

/*

$y = AC' + BC'D' + ABD'$

in0[1] = A

in0[0] = B

in1[1] = C

in1[0] = D

*/

wire w1, w2, w3;

assign w1 = in0[1] & (~in1[1]);

assign w2 = in0[0] & (~in1[1]) & (~in1[0]);

assign w3 = in0[1] & in0[0] & (~in1[0]);

assign comp = w1 | w2 | w3;

endmodule

8 Bit Greater than or Equal

`timescale 1ns / 1ps

//tests A >= B

```
module bit8_GEQ(input [7:0] A, input [7:0] B, output res);
```

```
    wire eq1_out, eq2_out, eq3_out, eq4_out, res_eq;
```

```
    wire gth1_out, gth2_out, gth3_out, gth4_out, res_gth;
```

```
    eq2 equalA(.a(A[7:6]), .b(B[7:6]), .aeqb(eq1_out)); //Aeq
```

```
    eq2 equalB(.a(A[5:4]), .b(B[5:4]), .aeqb(eq2_out)); //Beq
```

```
    eq2 equalC(.a(A[3:2]), .b(B[3:2]), .aeqb(eq3_out)); //Ceq
```

```
    eq2 equalD(.a(A[1:0]), .b(B[1:0]), .aeqb(eq4_out)); //Deq
```

```
    assign res_eq = eq1_out & eq2_out & eq3_out & eq4_out;
```

```
    bit2_GTH GTHA(.in0(A[7:6]), .in1(B[7:6]), .comp(gth1_out)); //A
```

```
    bit2_GTH GTHB(.in0(A[5:4]), .in1(B[5:4]), .comp(gth2_out)); //B
```

```
    bit2_GTH GTHC(.in0(A[3:2]), .in1(B[3:2]), .comp(gth3_out)); //C
```

```
    bit2_GTH GTHD(.in0(A[1:0]), .in1(B[1:0]), .comp(gth4_out)); //D
```

```
    assign res_gth = gth1_out | (gth2_out & eq1_out) | (gth3_out & eq2_out & eq1_out) | (gth4_out  
& eq3_out & eq2_out & eq1_out);
```

```
    assign res = res_eq | res_gth;
```

```
endmodule
```

2 Bit Equal Testbench

```
`timescale 1 ns/10 ps
```

```
module testbench;

    // signal declaration
    reg [1:0] test_in0, test_in1;
    wire test_out;
    integer vec1, vec2;

    // instantiate the circuit under test
    bit2_GTH uut (.in0(test_in0), .in1(test_in1), .comp(test_out));

    // test vector generator
    initial
    begin
        $monitor("Vec 1: %2b, Vec 2: %2b, Output: %1b", test_in0, test_in1, test_out);
        // test_in0 = 2'b10;
        // test_in1 = 2'b10;
        for(vec1=2'b00;vec1<=2'b11;vec1=vec1+1)begin
            for(vec2=2'b00;vec2<=2'b11;vec2=vec2+1)begin
                test_in0 = vec1;
                test_in1 = vec2;
                #200;
            end
        end
    end
endmodule
```

8 Bit Greater Than or Equal

`timescale 1ns / 1ps

```
module bit8_GEQ_tb;
    reg [7:0] test_in0, test_in1;
    integer vec1, vec2;
    wire result;
    bit8_GEQ gate(.A(test_in0), .B(test_in1), .res(result));

    initial begin
        for(vec1=8'b00000000;vec1<=8'b11111111;vec1=vec1+1)begin
            for(vec2=8'b00000000;vec2<=8'b11111111;vec2=vec2+1)begin
                test_in0 = vec1;
                test_in1 = vec2;
                #200;
            end
        end
    end
endmodule
```